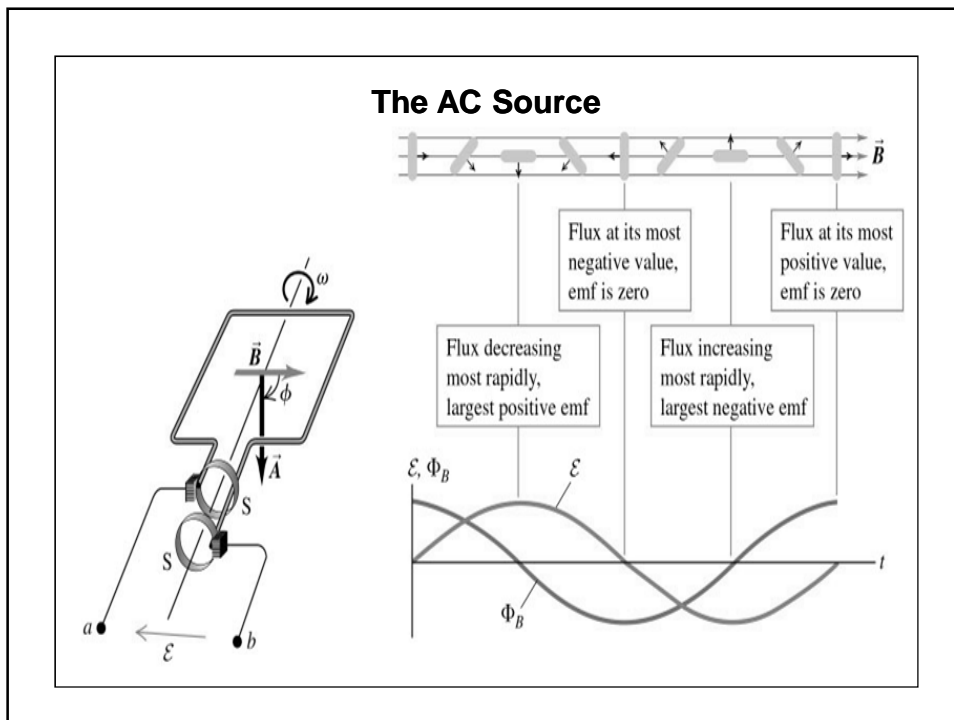


# General Physics II

## AC Circuits




### Oscillating Current and Voltage

Output voltage appears at the terminals and is sinusoidal in time with an angular frequency  $\omega$ .

$$V(t) = V_{\max} \sin(\omega t)$$

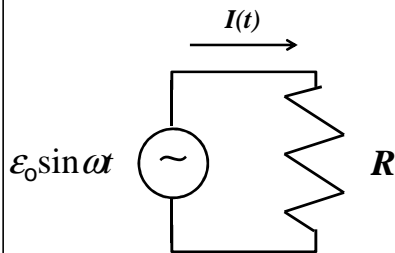- Recall that,  $\omega = 2\pi f$  where  $f$  is the frequency in Hertz (Hz)
- In the US and the rest of the Western Hemisphere, the frequency is 60 Hz.





Oscillating circuits have both AC voltage and current.

For resistors this is:

$$I(t) = \frac{\varepsilon_0}{R} \sin(\omega t)$$

### Simple AC Circuits -- Resistor



Resistor connected to ac source

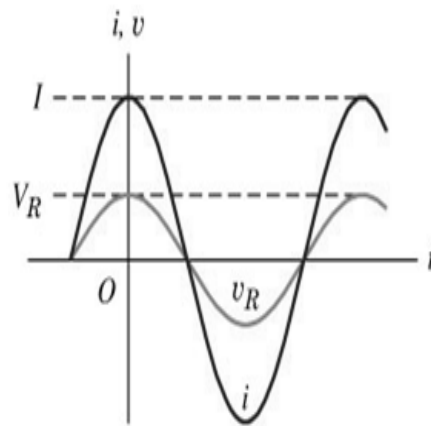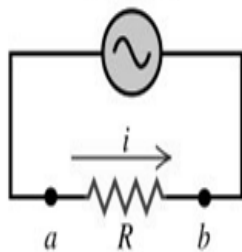

This is sometimes called a "resistive load" on the circuit

### Simple AC Circuits -- Capacitor

Capacitor connected to ac source

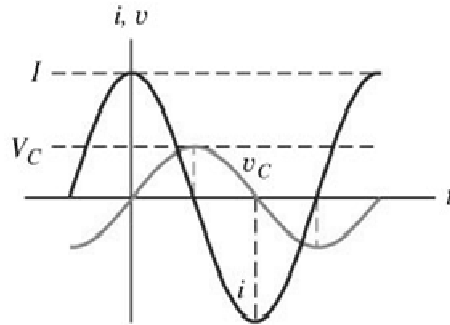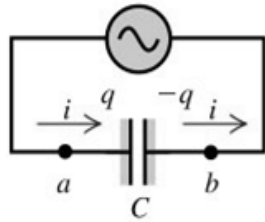

For symmetry reasons, we introduce "capacitive reactance",  $X_C$ :

$$X_C = \frac{1}{\omega C}$$

$$V_{\max} = I_C X_C$$

Capacitive reactance has units of ohms

### Impedance, Z

- The impedance of the circuit is the effective resistance
  - ◀ Has units of ohms
  - ◀ Consists of
    - » Total resistance, R
    - » Total capacitance, C
- $V=IZ$ , amplitude of voltage across AC circuit

$$V^2 = V_C^2 + V_R^2$$

$$V^2 = I^2 [X_C^2 + R^2]$$

$$I = \frac{V}{\sqrt{X_C^2 + R^2}}$$

$$Z = \sqrt{X_C^2 + R^2}$$


### Root Mean Square (RMS)

- The value of an AC voltage is continually changing from zero up to the positive peak, through zero to the negative peak and back to zero again.
- Instead we use the **root mean square voltage** ( $V_{\text{RMS}}$ ):

$$V_{\text{RMS}} = \frac{V_{\text{max}}}{\sqrt{2}}$$

- These equations also apply to **current**:
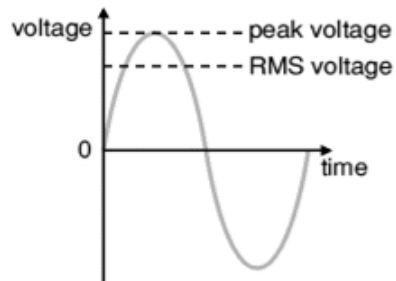
$$I_{\text{RMS}} = \frac{I_{\text{max}}}{\sqrt{2}}$$



- The RMS value is the **effective value of a varying voltage or current. It is the equivalent steady DC (constant) value which gives the same effect.**

**End of  
AC Circuits  
Lecture**